

Table of Contents

Chapter 1: General	1
1.1 Introduction	1
1.2 Structure of an Atom	2
1.3 Electric Charge and Current	3
1.4 Electromotive Force and Current.....	3
1.5 Electric Potential and Potential Difference	4
1.6 Electromotive Force and Potential Difference.....	5
1.7 Resistance	5
1.8 Specific Resistance or Resistivity	5
1.9 Conductance	6
1.10 Conductivity	6
1.11 Effect of Temperature on Resistance	6
Effect of Temperature on Pure Metals.....	6
Effec of Temperature on Alloys.....	7
Effect of Temperature on Insulators	7
Effect of Temperature on Semiconductors.....	8
1.12 Resistance Temperature Coefficient (RTC).....	8
Effect of Temperature on Resistance Temperature Coefficient (RTC).....	10
1.13 Effect of Temperature on Resistivity	12
1.14 Resistance of Temperature Coefficient (RTC) of Composite Conductor	12
1.15 Insulation Resistance	14
Expression for Insulation Resistance of Cable.....	14
1.16 Effect of Temperature on Insulating Material.....	16
1.17 Effect of Moisture on Insulating Material.....	16

1.18	SI units of Work, Power and Energy	17
	SI units for Mechanical system	17
	SI Units for Thermal System	19
	SI Units for Electrical System	20
1.19	Batteries and Cells	21
1.20	Classification of Cells	22
1.21	Lead-Acid Cell	22
	Construction of a Lead-Acid Cell	23
	Applications of the Lead-Acid Battery	25
	Indications of Charged Lead-Acid Cell	25
	Maintenance Measures for the Lead-Acid Car Batteries	25
	Trickle-charging in Lead-Acid Car Batteries	26
	Boost-Charging in Lead-Acid Car Battery	26
	Battery Maintenance	26
1.22	Nickel-Metal Hydride (Ni-MH) Battery	26
	Construction of Nickel-Metal Hydride Battery	27
	Advantages of the Nickel-Metal Hydride Battery	28
	Disadvantages of the Nickel-Metal Hydride Battery	28
	Application of Nickel-Metal Hydride (Ni-MH) Battery	28
1.23	Nickel-Cadmium Cell	28
	Components of the Nickel Cadmium Cell	29
	Chemical Reaction	30
	Advantages of the Nickel Cadmium Cell	30
	Disadvantages of the Nickel Cadmium Cell	30
	Application of Nickel Cadmium Cell	30
1.24	Methods of Charging the Storage Batteries	31
	Constant-Voltage Method	31
	Constant-Current Method	31
	The Rectifier Method	32

1.25	Combination of Batteries.....	32
	Series Combination.....	33
	Parallel Combination.....	33
	Series - Parallel Combination.....	34
1.26	Comparison between Various Batteries.....	35
	Summary.....	36
	Problems	37
	Problems on Insulation Resistance.....	37
	Problems on Fundamentals of Electricals (RTC).....	43
	Problems on Thermal Energy	58
	Problems on Mechanical Energy	62
	Problems on Electrical Energy	70
	Questions	73
Chapter 2: D.C Circuits		75
2.1	Introduction	75
2.2	Circuit Terminology.....	75
2.3	Classification of Electrical Network	76
2.4	Energy Sources	76
	Independent Source.....	77
	The Dependent Source.....	78
2.5	The Ohm's Law	79
	Series Circuit.....	79
	Parallel Circuit	80
2.6	Delta to Star and Star to Delta Transformation.....	80
	Delta to Star Transformation.....	81
	Star to Delta Transformation.....	82
2.7	Kirchhoff's Law	84
	Kirchhoff's Current Law (KCL).....	84
	The Kirchhoff's Voltage Law (KVL)	84

2.8	The Cramers Rule.....	86
2.9	Current Division.....	87
2.10	Voltage Division.....	88
2.11	Open Circuit and Short Circuit.....	88
2.12	The Superposition Theorem.....	89
2.13	The Thevenins Theorem.....	90
2.14	The Nortons Theorem.....	91
2.15	The Maximum Power Transfer Theorem.....	91
2.16	Source Transformation.....	93
2.17	Redundant Branches.....	95
	Summary.....	95
	Problems.....	96
	Problems on Star-Delta Transformation.....	96
	Problems Based on Kirchhoff's Law.....	120
	Problems Based on Superposition Theorem.....	135
	Problems based on Thevenins Theorem.....	163
	Problems based on the Norton's Theorem.....	197
	Problems based on Maximum Power Transfer.....	198
	Problems based on Redundant Branch.....	209
	Problems Based on Source Transformations.....	212
	Questions.....	220

Chapter 3: Magnetic Circuits221

3.1	Introduction.....	221
3.2	Magnet.....	222
3.3	Magnetic Induction.....	222
	Laws of Magnetism.....	222
3.4	Magnetic Field.....	223
3.5	Magnetic Lines of Force.....	223

3.6	Magnetic Flux (ϕ).....	224
3.7	Pole Strength.....	224
3.8	Magnetic Flux Density (B).....	224
3.9	Magnetic Field Strength (H)	224
3.10	Magnetic Effects of an Electric Current.....	225
	Electromagnetism Due to Straight Conductor Carrying Current.....	225
	Rules for Direction of Magnetic Field.....	226
3.11	Right Hand Thumb Rule.....	227
3.12	Nature of Magnetic Field Due to Long Straight Conductor	228
3.13	Force on a Current Carrying Conductor in a Magnetic Field	229
	Fleming's Left Hand Rule.....	229
	Magnitude of Force Experienced by a Conductor	230
3.14	Force Between Two Parallel Current Carrying Conductors	231
3.15	Expression for the Force Experienced by Two Long Straight Parallel Conductors.....	232
3.16	Permeability	233
	Absolute Permeability.....	233
	Permeability of Free Space or Vacuum	233
	Relative Permeability	234
3.17	Magneto Motive Force (mmf).....	234
3.18	Reluctance (S).....	234
3.19	Permeance	235
3.20	Magnetic Circuit.....	235
3.21	Series or Composite Magnetic Circuits	236
3.22	Parallel Magnetic Circuits.....	237
	Parallel Magnetic Circuit with Air Gap.....	239
3.23	Kirchhoff's Laws for Magnetic Circuits	239
	Kirchhoff's Flux Law.....	240
	Kirchhoff's MMF Law	240

3.24	Comparison Between Electric and Magnetic Circuits.....	240
3.25	Magnetic Leakage and Fringing.....	241
	Summary.....	242
	Problems	243
	Questions	270

Chapter 4: Electromagnetic Induction.....271

4.1	Introduction	271
4.2	Faraday’s Laws of the Electromagnetic Induction	271
4.3	Direction of Induced emf	273
	Fleming’s Right Hand Rule.....	273
	Lenz’s Law.....	274
4.4	Nature of Induced E.M.F.....	275
	Dynamically Induced emf.....	275
	Statically Induced emf.....	276
4.5	Self-Induced emf	276
	Expression for Magnitude of Self-Induced emf	277
	Coefficient of Self-Induction	278
	Factors Affecting Inductance of Coil.....	279
4.6	Mutually Induced EMF	279
	Expression of Magnitude of Mutually Induced emf	280
	Coefficient of Mutual Induction	281
	Coefficient of Coupling or Magnetic Coupling Coefficient.....	282
	Inductance of Inductively-Coupled Coils in Series	283
4.7	Energy Stored in the Magnetic Field	284
	Expression for Energy Stored in the Magnetic Field	285
	Energy Stored Per Unit Volume	286
4.8	Eddy Current Loss	286
4.9	Example of Coefficient of Coupling	287

Summary.....	288
Problems	289
Questions	305
Chapter 5: Electrostatics	307
5.1 Introduction	307
5.2 Electric Charge.....	308
5.3 Coulomb's Law.....	308
5.4 Electric Field.....	310
5.5 Electric Lines of Force	310
5.6 Electric Field Strength or Field Intensity	311
5.7 Electric Flux.....	311
5.8 Electric Flux Density	312
5.9 Surface Charge Density	312
5.10 Electric Potential.....	312
5.11 Potential Difference.....	313
5.12 Potential Gradient	313
5.13 Permittivity	314
Absolute Permittivity.....	314
Permittivity of Free Space.....	314
Relative Permittivity	314
5.14 Capacitor and its Capacitance	314
Action of a Capacitor.....	315
5.15 Relation Between Charge and Applied Voltage	316
5.16 Dielectric Strength and Breakdown.....	316
5.17 Capacitors in the Series Combination	316
5.18 Capacitors in the Parallel Combination	317
5.19 Types of Capacitors.....	318
5.20 Capacitance of a Parallel Plate Capacitor	319

5.21	Capacitance of a Parallel Plate Capacitor with Multiple Plates.....	320
5.22	Composite Dielectric Capacitors.....	320
	Series Composite Capacitor	321
	Parallel Composite Capacitor	322
	Series and Parallel Composite Capacitor	323
5.23	Energy Stored in a Capacitor	324
5.24	Charging of a Capacitor	325
	Mathematical Expression	326
	Initial Charging Current.....	328
	Time Constant (For Charging).....	329
5.25	Discharging of a Capacitor	329
	Mathematical Expression	331
	Initial Discharging Current	333
	Time Constant (for Discharging).....	333
	Summary.....	334
	Problems	334
	Questions	343

Chapter 6: A.C Fundamentals345

6.1	Introduction	345
6.2	Generation of Alternating Current and Voltage.....	346
6.3	Important Definitions	349
6.4	Equation of an Alternating Quantity.....	349
6.5	Root Mean Square (R.M.S) Value of Alternating Quantity	351
	Graphical Method.....	351
	Analytical Method.....	352
6.6	Average Value of Alternating Quantity.....	354
	Graphical Method.....	354
	Analytical Method.....	355

6.7	Form Factor	356
6.8	Peak Factor, Crest Factor, or Amplitude Factor.....	356
6.9	Phase	357
6.10	Positive Phase	358
6.11	Negative Phase	358
6.12	Inphase.....	358
6.13	Phase Difference	359
	Leading Phase Difference	359
	Lagging Phase Difference.....	359
6.14	Phasor Diagram.....	360
6.15	Addition and Subtraction of Phasor.....	360
6.16	Representation of Phasors.....	361
6.17	Multiplication and Division of Phasor.....	362
6.18	Exponential Form of Phasor Representation.....	363
	Summary.....	363
	Problems	364
	Questions	385
Chapter 7: Single Phase A.C Circuits		387
7.1	Introduction	387
7.2	Pure Resistive A.C Circuit.....	387
	Power.....	388
7.3	Pure Inductive A.C Circuit	389
	Power.....	391
	Inductive Reactance (X_L).....	392
7.4	Pure Capacitive A.C Circuit	392
	Power.....	393
	Capacitive Reactance (X_C).....	394
7.5	Series R-L, A.C Circuit.....	394

	Impedance (Z)	395
	Power	396
	Power Triangle and its Components	397
	Power Factor	397
7.6	Series R-C, A.C Circuit	398
	Impedance (Z)	399
	Power	400
	Power Triangle and its Components	400
7.7	Series R-L-C, A.C Circuit.....	401
	Impedance (Z)	402
	First Condition, $X_L > X_C$	402
	Power Triangle	404
	Second Condition, $X_C > X_L$	404
	Power Triangle	405
	Third Condition, $X_L = X_C$	405
	Characteristics of Resonance in Series R-L-C Circuit	406
	Expression for Resonant Frequency.....	407
	Bandwidth of a Resonant Circuit	407
	Quality Factor of Series Circuit.....	408
7.8	Parallel A.C Circuit	408
	Characteristics of Resonance in Parallel R-L-C Circuit	409
	Expression for Resonant Frequency in Parallel Circuit.....	411
7.9	Dynamic Impedance at Resonance	411
7.10	Admittance.....	412
	Quality Factor of Parallel Circuit.....	413
7.11	Multiplication and Division of Impedances.....	414
7.12	Addition and Subtraction of Impedances.....	414
	Summary.....	415
	Problems	415
	Questions	466

Chapter 8: Polyphase A.C Circuits.....	467
8.1 Introduction	467
8.2 Advantages of Polyphase (Three-Phase) over Single-Phase System	467
8.3 Generation of Three-Phase Voltages	468
Symmetrical System	469
Phase Sequence	469
Balanced Load	469
8.4 Three-phase Interconnection System	469
Star or Wye Connection Type	469
Delta or Mesh Connection Type	473
Summary.....	477
Problems	477
Polyphase (3- ϕ) Circuit.....	477
Questions	496
Chapter 9: Single Phase Transformer	497
9.1 Introduction	497
9.2 Principal of Working.....	497
9.3 Construction.....	498
9.4 Types of Transformers.....	500
9.5 E.M.F. Equation of a Transformer.....	502
Voltage Ratio (K) of Transformer	503
Current Ratio (K) of Transformer.....	503
9.6 Volt-Ampere Rating of Transformer	504
Ideal Transformer	504
Ideal Transformer on No-load	505
9.7 Practical Transformer on No-load	505
9.8 Leakage Reactance	507
9.9 Practical Transformer On-Load.....	507

9.10	Equivalent Parameters.....	508
	Equivalent Resistance	508
	Equivalent Leakage Reactance.....	510
	Equivalent Impedance	510
9.11	Transformer Losses.....	510
9.12	Transformer Efficiency	512
	Condition for Maximum Efficiency	514
	Load Current at Maximum Efficiency	515
	Output VA Corresponding to Maximum Efficiency	515
	Maximum Efficiency of transformer.....	516
	Maximum Efficiency of a Transformer Considering Volt-ampere Rating ...	516
9.13	Voltage Regulation.....	517
9.14	Efficiency and Regulation of Transformer by Direct Loading Method.....	518
9.15	Auto-Transformer/Dimmerstat/Variac/Single winding Transformer	520
	Copper Saving in Auto-Transformer	521
	Summary.....	523
	Problems	523
	Questions	542
	Formulas	543
	Index	553