

Table of Contents

<i>Preface</i>	<i>iii</i>
Chapter 1: Diodes and Circuits	1
1.1 Introduction	1
1.2 Structure of an Atom.....	2
1.3 Classification of Solid Materials on the Basis of Conductivity	2
1.4 Atomic Bonds.....	3
1.5 Energy Band Theory	4
1.6 Semiconductors	5
Intrinsic Semiconductors	5
Extrinsic Semiconductors.....	7
1.7 p-n Junction.....	10
Formation of Depletion Region.....	10
Barrier Potential	13
Biasing of a p-n Junction	13
1.8 p-n Junction Diode	17
V-I Characteristics of a p-n Junction Diode	18
Effect of Temperature on the Diode V-I Characteristics.....	21
Diode Equivalent Circuit Models	22
Using the Diode as a Rectifier	25
Filter Circuits	45
1.9 Zener Diode.....	48
V-I Characteristics of a Zener Diode	49
Equivalent Circuit of a Zener Diode.....	52
Breakdown Mechanisms in a Zener Diode	53
Specifications of a Zener Diode.....	55
Zener Diode Applications.....	55
1.10 Light Emitting Diode	57
Materials for LED.....	59
LED Characteristics	60
LED Display.....	61

	Multiplexed Display	67
	Summary	68
	Problems	69
	Multiple Choice Questions	69
	Solved Questions.....	72
	True or False	89
	Unsolved Questions.....	89
	Chapter 2: Semiconductor Devices and Applications	91
2.1	Introduction	91
2.2	Bipolar Junction Transistor	92
	Structure of BJT	92
	Working of a Transistor	94
	Current Components of a Transistor.....	94
	Performance Parameters of BJT	95
	Modes of Operation in BJT	97
	Configurations of BJT	99
	Static Characteristics of BJT	102
	Direct Current (DC) Analysis of a Transistor.....	106
2.3	DC Load Line Analysis.....	106
2.4	Concept of Amplification.....	108
	Amplifier Characters	108
	Voltage Amplifier	109
	Single Stage RC Coupled CE Amplifier.....	110
	Gain Bandwidth Product	111
	Frequency Response	112
	Applications of BJT	112
	Specifications of BJT	115
2.5	Field Effect Transistor.....	115
	Advantages of FET Over BJT.....	116
	Junction Field Effect Transistors (JFET)	116
	Metal-Oxide Semiconductor Field Effect Transistor (MOSFET)	122
2.6	Power Semiconductor Devices	127
	Silicon-Controlled Rectifier (SCR)	127
	Diode for Alternating Current (DIAC)	130
	Triode for Alternating Current (TRIAC)	132

Summary	134
Problems	135
Multiple Choice Questions	135
Solved Questions.....	139
True or False	145
Unsolved Questions.....	145
Chapter 3: OP-AMP and Applications.....	147
3.1 Introduction	148
3.2 The OP-AMP's Schematic Symbol and Pin Configuration.....	148
3.3 DC Power Supply for OP-AMP.....	149
3.4 The Ideal OP-AMP	150
The Ideal Differential Amplifier	150
The Differential Gain (A_d).....	151
The Common Mode Gain (A_c).....	151
The Common Mode Rejection Ratio (CMRR).....	152
3.5 Block Diagram of a Typical OP-AMP.....	153
3.6 The Ideal OP-AMP.....	154
3.7 The Equivalent Circuit of an OP-AMP	155
3.8 The Practical OP-AMP.....	156
Op-Amp applications	158
3.9 The 741 IC.....	158
The 741 IC Pin Configuration.....	158
Features of 741 IC.....	159
Packages of Op-Amp.....	159
The Characteristics of 741 IC	159
3.10 The Open Loop Configuration of OP-AMP (Comparator).....	159
3.11 The Closed Loop Configuration of OP-AMP	160
3.12 Gain with or without Feedback.....	161
3.13 The Negative Feedback and its Gain.....	161
The Advantages of Negative Feedback	162
The Applications of Negative Feedback	163
3.14 Negative Feedback Configuration	163
Comparing four types of feedback amplifiers	165
3.15 The Positive feedback and its Gain.....	166
The Applications of Positive Feedback	167

3.16	The Virtual Short	167
3.17	The Virtual Ground.....	168
3.18	The Zero input current	168
3.19	The Inverting Amplifier	168
	Applications of Inverting Amplifier.....	169
3.20	The Non-Inverting Amplifier	170
3.21	The Voltage Follower.....	171
	Advantages of the Voltage Follower.....	172
3.22	The Adder or Summing Amplifier	172
	The Inverting Adder or Inverting Summing Amplifier	172
	The Non-inverting adder or Non-inverting Summing Amplifier.....	173
	The Three Input Signals Non-inverting adder or Non-inverting Summing Amplifier.....	175
3.23	The Difference or Subtractor Amplifier	176
3.24	The Integrator	178
	The Input and Output Waveforms of Integrator Circuit.....	180
3.25	The Differentiator	182
	The Input and Output Waveforms of Differentiator Circuit	184
3.26	The Voltage-to-Current Converter (V to I)	186
	Applications of Voltage-to-Current Converter	187
3.27	The Current-to-Voltage Converter (I to V)	187
	Applications of Current-to-Voltage Converter	188
3.28	The OP-AMP Waveform Generator.....	188
3.29	The Barkhausen Criterion	189
3.30	The Square Wave Generator	189
	The Inverting Schmitt Trigger.....	189
	The Non-Inverting Schmitt Trigger.....	192
	The Astable Multivibrator	195
3.31	The Sine Wave Generator.....	197
	The RC Phase Shift Oscillator using OP-AMP	197
	The Wien's Bridge Oscillator using OP-AMP.....	198
3.32	The Triangular Wave Generator	199
	Summary	202
	Problems.....	202
	Multiple Choice Questions	202
	Solved Questions.....	205

True or False	208
Unsolved Questions.....	209
Chapter 4: Digital Electronics.....	211
4.1 Introduction	211
4.2 Positive and Negative Logic	212
4.3 Logic Operations and Operators.....	213
The NOT Logic Operator	213
The AND Logic Operator	213
The OR Logic Operator	214
4.4 Logic Gates.....	215
The NOT Gate.....	215
The AND Gate.....	216
The OR Gate.....	217
The NAND Gate.....	219
The NOR Gate	220
The Exclusive-OR Gate.....	222
The Exclusive-NOR Gate	223
4.5 Universal Gates.....	225
4.6 The Boolean Algebra.....	225
Laws of Boolean Algebra	226
The DeMorgan's Theorems	227
4.7 Duality	229
4.8 The Digital ICs Logic Families.....	229
4.9 Integrated Circuit Technology.....	231
4.10 The Logic Circuits	232
4.11 The Binary Adder.....	233
The Half Adder	233
The Full Adder	235
4.12 The Multiplexer	238
The 2:1 Multiplexer.....	239
The 4:1 Multiplexer.....	240
4.13 The Demultiplexer.....	242
The 1:2 Demultiplexer	243
The 1:4 Demultiplexer	244
4.14 The Flip-Flop.....	246

	The Clock Pulse	246
	The Set-Reset Flip-Flop	246
	The Clocked SR Flip-Flop	248
	The JK Flip-Flop	249
	The D Flip-Flop	250
4.15	Shift Register	251
	Serial Shift-Left Register.....	253
	Serial Shift-Right Register.....	255
	SIPO Shift Register.....	255
	PISO Shift Register.....	255
	PIPO Shift Register	256
4.16	Counters	257
	Asynchronous Counter (Ripple-Up Counter).....	258
	Synchronous Counter.....	259
	Ripple-Down Counter.....	260
4.17	The Microprocessor.....	260
4.18	The Microcontroller.....	263
	Advantages of Microcontroller and Microprocessor	265
	Applications of Microcontroller and Microprocessor	265
	Comparison between Microcontroller and Microprocessor	265
	Summary	266
	Problems	267
	Multiple Choice Questions	267
	Solved Problems.....	269
	True and False	301
	Unsolved Questions.....	301
	Chapter 5: Industrial Applications of Electronic Devices.....	303
5.1	Introduction	303
5.2	Transducers.....	304
	Temperature Transducers.....	304
	Level Transducers.....	306
	Displacement Transducers	307
	Pressure Transducers	308
5.3	Digital Thermometer.....	313
5.4	Weighing Machine	314
5.5	Two-Wire Transmitters	315

5.6	PID Controllers	316
	Control Loop Action	317
	Action Modes of a PID Controller	317
	Working Principle of a PID Controller	317
	Tuning a Control Loop	320
	Advantages of a PID Controller	321
	Limitations of a PID Controller	321
	Applications of a PID Controller	322
5.7	Data Loggers	322
	Types of Data Loggers	322
	Data Logging Techniques	322
	Differences between Data Logging and Data Acquisition	323
	Applications of Data Loggers	323
5.8	Alarm Annunciator	324
	Principle of operation	324
	Special Function Modules	326
5.9	NC Machine	327
5.10	CNC Machine	328
	Axis of Motion of a CNC Machine	330
	Applications of a CNC Machine	331
5.11	Programmable Logic Controller (PLC)	331
	Components of PLC	331
	Working Principle of PLC	333
	Advantages and Disadvantages of a PLC	333
	Differences between a PLC and a Computer	334
	Summary	334
	Problems	334
	Multiple Choice Questions	334
	True or False	337
	Unsolved Question	337
Chapter 6: Communication Systems		339
6.1	Introduction to Communication System	339
6.2	Elements of a Communication System	340
	Transmitter	340
	Communication Channel	341

	Receiver	341
	Noise	341
6.3	Classification of the Electronic Communication Systems.....	341
	On the Basis of Modes of Transmission.....	341
	On The Basis of Nature of signal	342
	On the Basis of Transmission Technique.....	343
6.4	IEEE Frequency Spectrum Used in Communication Systems	343
	Frequency Bands	344
	Units of Measurement and Abbreviations	347
	Bandwidth and Other Parameters.....	347
	Spectrum Assignment and Regulation	349
6.5	Modulation.....	349
	Amplitude Modulation	350
	Frequency Modulation.....	355
6.6	Basics of Transmitters	359
	Continuous-Wave Transmitter	359
	AM Transmitter.....	360
	Methods to Generate FM Waves.....	361
6.7	Radio Receivers	365
	Types of Radio Receivers.....	365
6.8	Communication Media and Its Classification	367
	Guided Propagation	367
	Unguided Propagation.....	376
	Summary	381
	Problems	381
	Multiple Choice Questions	381
	Solved Questions.....	385
	State true or false.....	389
	Unsolved Questions.....	389
	Miscellaneous Questions	391
	Answers	409
	About the CD.....	415
	Index.....	431
	Test Paper	437